

## What is a relay?

GPIO15

GPIO18

GPIO23

GPI024

GPIO25

GPIO8 SPIO CEO I

GPI07

ID\_SC

Ground

GPIO12

Ground

GPIO17

GPIO27

GPI022

GPIO10 SPI0\_MOSI

GPI09

GPI011

Ground

ID SD

GPI05

GPI06

GPIO13

13 14

17 18

19 20

23 24

**25 26** 

29 30

31 32

33 34

35 (36)

39 (40)

15 16

21


27 28


A relay is an electro magnetic switch that can handle a larger load than the raspberry pi can power by itself.

In this case that is a high voltage AC load (alternating current) Connecting this to the Pi would certainly fry it.. In fact, connecting this to us could fry us also!

Be careful and unplug your machine before wiring and have an adult present to double check your connections before testing.

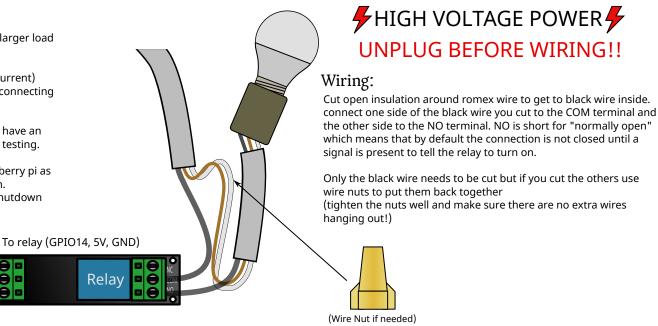
This setup is using the GPIO serial port pin on the raspberry pi as a signal to turn on the relay causing the light to turn on. Once the Raspberry Pi turns off the serial port is also shutdown causing the light to turn off.



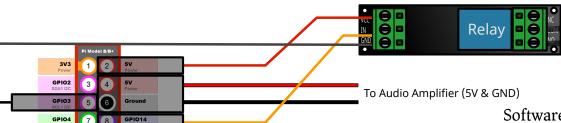
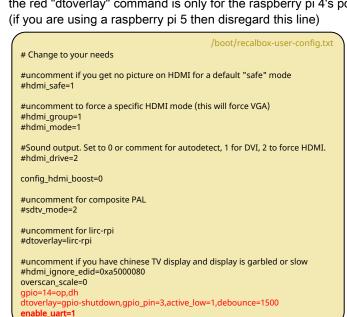
## Software Configuration:

On the SD card in the raspberry pi there is a partition named boot. there you will find a file named: recalbox-user-config.txt we need to add the "enable\_uart=1" to the bottom of the file. the red "dtoverlay" command is only for the raspberry pi 4's power switches (if you are using a raspberry pi 5 then disregard this line)



## Notice!

The GND and 5V connections may be different on your board from what is shown here. The exact pin location doesnt matter so long as the connections are correct.

To Rpi 4 power switch

(GPIO3 & GND)

All GND pins are connected together and both 5V lines are also connected.

The important thing to pay attention to is that 5V and GND are not mixed up and that the GPIO pins are connected to the header where they need to be.

GPIO14 = relay in GPIO3 = power switch (rpi 4 only)